




CHAPTER-6

Arithmetic Unit

Shift-add multiplication:

=> multiplication of unsigned numbers.

 => multiplication can be performed by repeated addition of multiplicand and shifting



Contd...

C	A	Q	M	Initial Values	
0	0000	1101	1011		
0	1011	1101	1011	Add	} First Cycle
0	0101	1110	1011	Shift	
0	0010	1111	1011	Shift	} Second Cycle
0	1101	1111	1011	Add	
0	0110	1111	1011	Shift	} Third Cycle
1	0001	1111	1011	Add	
0	1000	1111	1011	Shift	} Fourth Cycle

RTL code for shift-add multiplication

```
1:     $C \leftarrow 0, U \leftarrow 0, i \leftarrow n$   
 $Y_0$  2:     $CU \leftarrow U + X$   
2:     $i \leftarrow i - 1$   
3:    shr(CUV), cir(Y)  
 $Z'$  3:    GOTO 2  
 $Z$  3:     $FINISH \leftarrow 1$ 
```

Contd...

Example $UV \leftarrow X \times Y$; $X = 1101$ and $Y = 1011$.


Conditions	Micro-operations	i	C	U	V	Y	Z	FINISH
START		x	x	xxxx	xxxx	1011		0
1	$C \leftarrow 0, U \leftarrow 0, i \leftarrow 4$	4	0	0000			0	
$Y_0 Z_2$	$CU \leftarrow U + X,$ $i \leftarrow i - 1$	3	0	1101			0	
3, Z' 3	shr(CUV), cir(Y), GOTO 2		0	0110	1xxx	1101		
$Y_0 Z_2$	$CU \leftarrow U + X,$ $i \leftarrow i - 1$	2	1	0011			0	
3, Z' 3	shr(CUV), cir(Y), GOTO 2		0	1001	11xx	1110		
2	$i \leftarrow i - 1$	1					0	
3, Z' 3	shr(CUV), cir(Y), GOTO 2		0	0100	111x	0111		
$Y_0 Z_2$	$CU \leftarrow U + X,$ $i \leftarrow i - 1$	0	1	0001			1	
3, Z 3	shr(CUV), cir(Y), FINISH $\leftarrow 1$		0	1000	1111	1011		1



Booth Algorithm

- It reduces the number of addition.
- Negative multiplier, positive multiplier are treated the same.
- For negative numbers multiplication, the operation is performed by representing the negative numbers in it's 2's complement form.
- **ADVANTAGES:**
 - => When there are lot of ones, all will be cancelled and replaced with zeros.
 - => More zeros means, it reduces the addition(no operation is done with zeros)
 - => But shift remains the same, can't be reduced.

Contd...

 

Multiply 9 x 3 using booth algorithm.

$(9)_{10} = (01001)_2$
 $M = 01001$
 $(+3)_{10} = (00011)_2$
 $(-3)_{10} = 11100$
 $\quad \quad \quad +1$
 $\quad \quad \quad 11101$
 $\text{i.e. } (-3)_{10} = (11101)_2 = \bar{Q}$

A	Q	Q ₋₁	Add(M)	Sub($\bar{M}+1$)	count	Remarks
00000	11101	0	01001	10111	5	Initialization
10111	11101	0	—	—	—	$A \leftarrow A - M$
11011	11110	1	—	—	4	Ans. of A, Q, Q ₋₁
21111 carry (first) 2101 discard 2101						
00100	11110	1	—	—	—	$A \leftarrow A + M$
00010	01111	0	—	—	3	Ans. of A, Q, Q ₋₁
11001	01111	0	—	—	—	$A \leftarrow A - M$
11100	10111	1	—	—	2	Ans. of A, Q, Q ₋₁
11110	01011	1	—	—	1	Ans. of A, Q, Q ₋₁
11111	00101	1	—	—	0	Ans. of A, Q, Q ₋₁

NOTE: MSB of A is preserved (for sign preservation)

Contd...

➤ Result Verification:

1 1 1 1 1 0 0 1 0 1

Since there is end around carry, we find it's 2's complement and place '-' sign before the equivalent decimal.

i.e. 0 0 0 0 0 1 1 0 1 1

i.e. -27

RTL code for Booth algorithm

```
1:  U <- 0, Y-1 <- 0, I <- n
Y0Y-1'2: U <- U + X' + 1
Y0'Y-12: U <- U + X
2:  i <- i - 1
3:  ashr(UV), cir(Y), Y-1 <- Y0
Z'3: goto 2
Z3:  FINISH <- 1
```

Perform 9×-3 multiplication using Booth algorithm.

Here,

$X = 9 = 01001$

$Y = -3 = 11101$

conditions	microoperations	i	U	V	Y	$Y_{-1}/2$	FINISH
START		x	xxxxxx	xxxxxx	11101	x	0
1	$U \leftarrow 0, Y_{-1} \leftarrow 0, i \leftarrow n$	5	00000			0	0
$Y_0 Y_{-1} 2, 2$	$U \leftarrow U + X' + 1$ $i \leftarrow i - 1$	4	10111			0	
$3, 2, 3$	$\text{ashr}(UV), \text{cir}(Y), Y_{-1} \leftarrow Y_0$ goto 2		11011	1xxxx	11110	1	
$Y_0 Y_{-1} 2, 2$	$U \leftarrow U + X$ $i \leftarrow i - 1$	3	00100			0	
$3, 2, 3$	$\text{ashr}(UV), \text{cir}(Y), Y_{-1} \leftarrow Y_0$ goto 2		00010	01xxx	01111	0	
$Y_0 Y_{-1} 2, 2$	$U \leftarrow U + X' + 1$ $i \leftarrow i - 1$	2	11001			0	
$3, 2, 3$	$\text{ashr}(UV), \text{cir}(Y), Y_{-1} \leftarrow Y_0$ goto 2		11100	101xx	10111	1	
2	$i \leftarrow i - 1$	1				0	
$3, 2, 3$	$\text{ashr}(UV), \text{cir}(Y), Y_{-1} \leftarrow Y_0$ goto 2		11110	0101x	11011	1	
2	$i \leftarrow i - 1$	0				1	
$3, 2, 3$	$\text{ashr}(UV), \text{cir}(Y), Y_{-1} \leftarrow Y_0$		11111	00101	11101	1	1

Here, $UV = 1111100101$

There is end around carry so, we find 2's complement and place '-ve' sign before the equivalent decimal.

-0000011011
i.e. -27

Shift subtract division

(Before we look at the operation of the entire algorithm, consider the circumstances under which the first step terminates the algorithm. For $112 \div 7$ with $n=4$, $UV = 0111\ 0000$ and $X = 0111$. Since, $U \geq X$, the algorithm exists immediately. Had it proceeded, it should have produced a result of 16 (1 0000) and a remainder of 0. The value 1 0000 cannot be stored in a 4-bit register), this is the reason for the overflow.

```
G1:  FINISH ← 1, OVERFLOW ← 1
      2:  Y ← 0, C ← 0, OVERFLOW ← 0, i ← n
      3:  shl(CUV), shl(Y), i ← i - 1
(C + G)4:  Y0 ← 1, U ← U + X' + 1
      Z'4:  GOTO 3
      Z 4:  FINISH ← 1
```

Contd...

Trace of the RTL code for the operation $147 \div 13$.

Here, $U = 1001$, $V = 0011$, $X = 1101$ and $n=4$.

Trace of the RTL code for the shift-subtract division algorithm

Conditions	Micro-operations	i	C	U	V	Y	Z	FINISH
START		x	x	1001	0011	xxxx		0
1	NONE							
2	$Y \leftarrow 0; C \leftarrow 0,$ $OVERFLOW \leftarrow 0,$ $i \leftarrow 4$	4	0			0000	0	
3	$shl(CUV), shl(Y),$ $i \leftarrow i - 1$	3	1	0010	0110	0000	0	
$(C + G)4, Z'4$	$Y_0 \leftarrow 1,$ $U \leftarrow U + X' + 1,$ GOTO 3			0101		0001		
3	$shl(CUV), shl(Y),$ $i \leftarrow i - 1$	2	0	1010	1100	0010	0	
$Z'4$	GOTO 3							
3	$shl(CUV), shl(Y),$ $i \leftarrow i - 1$	1	1	0101	1000	0100	0	
$(C + G)4, Z'4$	$Y_0 \leftarrow 1,$ $U \leftarrow U + X' + 1,$ GOTO 3			1000		0101		
3	$shl(CUV), shl(Y),$ $i \leftarrow i - 1$	0	1	0001	0000	1010	1	
$(C + G)4, Z4$	$Y_0 \leftarrow 1,$ $U \leftarrow U + X' + 1,$ FINISH $\leftarrow 1$		0100	0100	1011	1011		1

Binary Coded Decimal(BCD)

Binary Coded Decimal BCD Numbers

Each decimal digit to be represented in BCD is converted into its 4 digit binary equivalent. The final number will consist of four times the number of original decimal digits.

As the decimal digits relating to 1010, 1011, 1100, 1101, 1110, 1111 do not exist these are invalid.

Decimal	Binary	BCD
0	0000 0000	0000 0000
1	0000 0001	0000 0001
2	0000 0010	0000 0010
3	0000 0011	0000 0011
4	0000 0100	0000 0100
5	0000 0101	0000 0101
6	0000 0110	0000 0110
7	0000 0111	0000 0111
8	0000 1000	0000 1000
9	0000 1001	0000 1001
10	0000 1010	0001 0000
11	0000 1011	0001 0001
12	0000 1100	0001 0010
13	0000 1101	0001 0011
14	0000 1110	0001 0100
15	0000 1111	0001 0101
16	0001 0000	0001 0110
17	0001 0001	0001 0111
18	0001 0010	0001 1000
19	0001 0011	0001 1001
20	0001 0100	0010 0000

BCD adder:


(When two decimal numbers are added, the maximum result is 19 => (9 + 9 + 1(carry)))

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

Contd...


(The condition for the correction and setting $c=1$ is:

$$c = k + z_8z_4 + z_8z_2 = 1)$$

 

Specialized Arithmetic hardware

1. PIPELINING

 

T_1 = time taken by non-pipelined unit to calculate 1 result. Requires $n \cdot T_1$ time to calculate n results.
Pipelined unit requires k time units, each of duration T_k , to move the first piece of data through the pipeline.
Because, additional data enters the pipeline during every cycle, it will output the remaining $n-1$ results during next $n-1$ cycles.
 $\Rightarrow$ thus, the pipelined unit requires $(k + n - 1)$ cycles, each of T_k time, to calculate same results.
The speedup can be calculated by the formula above.




Contd.....

- Data enters into a stage of the pipeline, which performs some arithmetic operations on those data.
- The results are then passed to next stage which performs its operation and so on until the final computation has been performed.
- Each stage performs only its specific function, no need to be capable of performing the task of any other stage.
- A pipeline does not speed up an individual computation. It improves the performance by overlapping computations where each stage can operate on different data simultaneously.
- The net effect is that output appears more quickly than in non-pipeline arithmetic unit, thereby increasing the throughput.

 
2. Lookup Tables:

- Any combinational circuit can be implemented by ROM is a lookup table.
- Inputs to the combinational circuit serve as the address input of the ROM.
- Data outputs of the ROM corresponds to the output of the combinational circuit.
- ROM is programmed with data such that the correct values are output for any possible input values.
- Consider a 4 x 1 ROM programmed to mimic a two input AND gate.



- By programming ROM with data shown, it outputs the same values as the AND gate for all possible values of X and Y.

 Contd..(a multiplier implemented using a lookup ROM)






Contd...

- Registers X and Y supply the address inputs to lookup ROM.
- Its outputs are the product of X and Y, and are routed to registers U and V.
- Each of 256 locations must contain the 8-bit product of X and Y.
- For example, location 1011 1101 contains the data 1000 1111, 143, the product of 1011(11) and 1101(13).
- Advantages:
 - => the hardware may be less complex than that of the original shift-add implementation.
 - => can multiply numbers more quickly than the shift-add hardware.
 - => However, size of the lookup ROM grows rapidly as the size of the operands increases.

 3. Wallace Tree

- Combinational circuit used to multiply two numbers.
- Instead of performing additions using standard parallel adder, Wallace tree uses carry save adder and only one parallel adder.
- Carry save adder can add 3 values simultaneously. However, it does not output a single result, but provides both sum and a set of carry bits as output.



- To form the final sum, S and C must be added together because carry bits do not propagate through the adder.

- To use a carry save adder to perform multiplication, we first calculate the partial product of the multiplication and input them to carry save adder.


 


Fig: Generating partial products for multiplication using Wallace tree.

 
A 3 x 3 multiplier constructed using carry save adder.



Contd..

A 4 x 4 Wallace tree multiplier.

 Example 4 bit multiplication:
1011 and 1110



Contd...

An 8 x 8 Wallace tree multiplier.

